

CS 315 Combinational Logic

Midterm

Digital Design

Digital - splitters, subcircuits

Auto grader

Midterm

High 100

Low 25

Avg 74


Final

Do better

$$\text{Midterm}_{\text{new}} = \frac{\text{Final} + \text{Midterm}_{\text{old}}}{2}$$

Final 90 Midterm 70
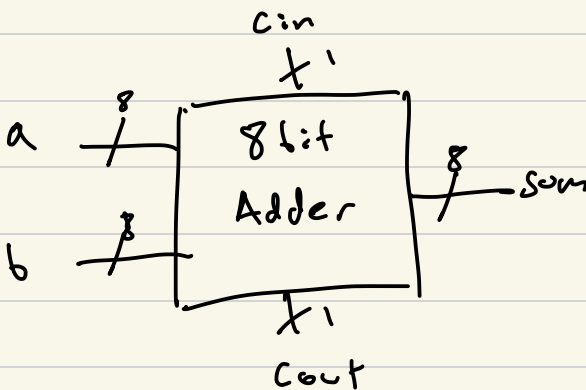
$$\text{Midterm}_{\text{new}} = \underline{80}$$



Ripple Carry Adder

Sum-of-products

A new function

3-bit number $n_2 n_1 n_0$ (bits)

Two 1-bit outputs: even odd

Goal: determine if the number of "1" bits are even or odd

110 even


111 odd

100 odd



| | n_2 | n_1 | n_0 | even | odd |
|---|-------|-------|-------|------|-----|
| ① | 0 | 0 | 0 | 1 | 0 |
| | 0 | 0 | 1 | 0 | 1 |
| | 0 | 1 | 0 | 0 | 1 |
| ② | 0 | 1 | 1 | 1 | 0 |
| | 1 | 0 | 0 | 0 | 1 |
| ③ | 1 | 0 | 1 | 1 | 0 |
| ④ | 1 | 1 | 0 | 1 | 0 |
| | 1 | 1 | 1 | 0 | 1 |

$$\text{even} = (\bar{n}_2 \cdot \bar{n}_1 \cdot \bar{n}_0) + (\bar{n}_2 \cdot n_1 \cdot n_0) \\ + (n_2 \cdot \bar{n}_1 \cdot n_0) + (n_2 \cdot n_1 \cdot \bar{n}_0)$$


$$\text{odd} = \overline{\text{even}}$$

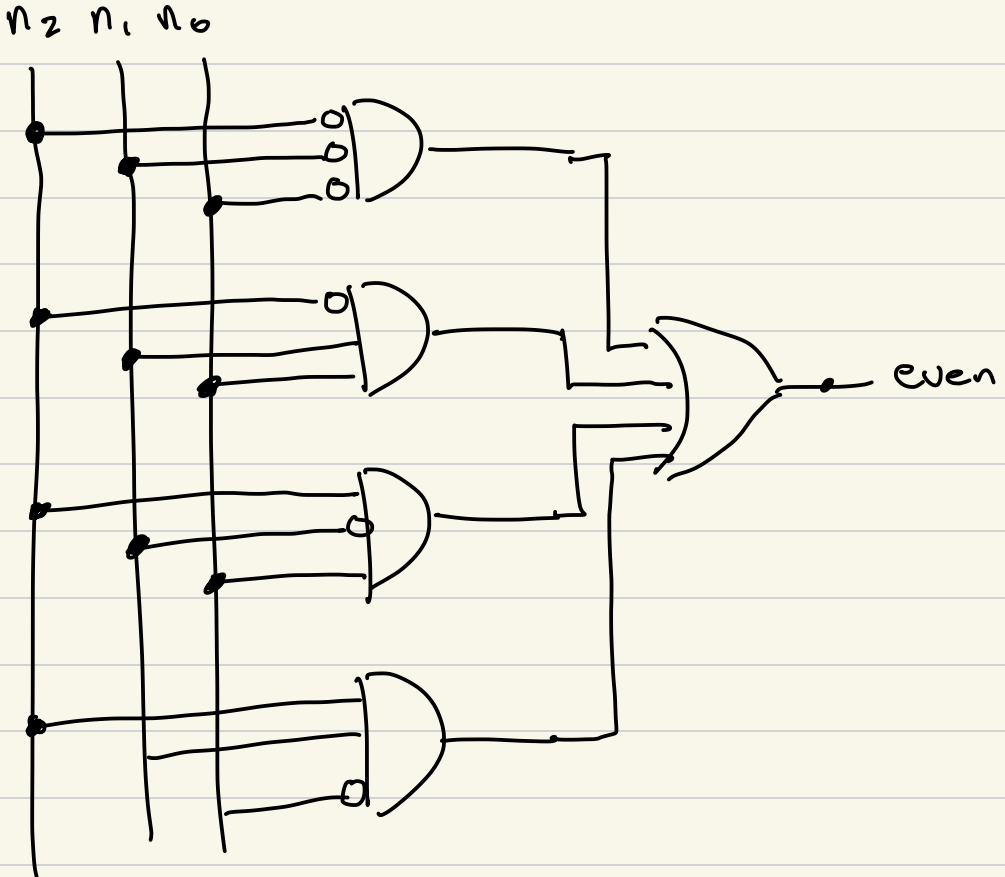


Lab 05 Part 2 max 2

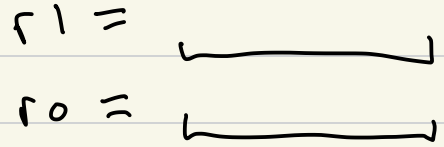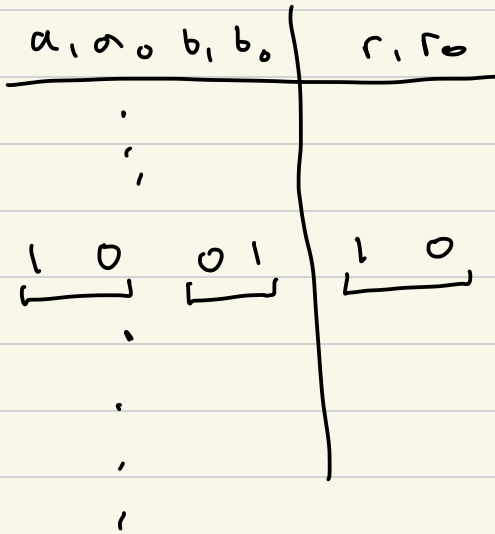

1 bit full adder

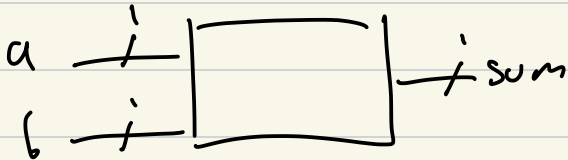


half adder

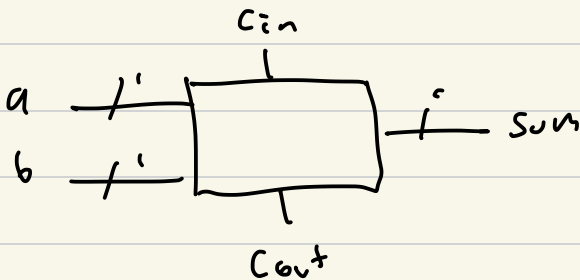


full adder

8 bit ripple-carry adder

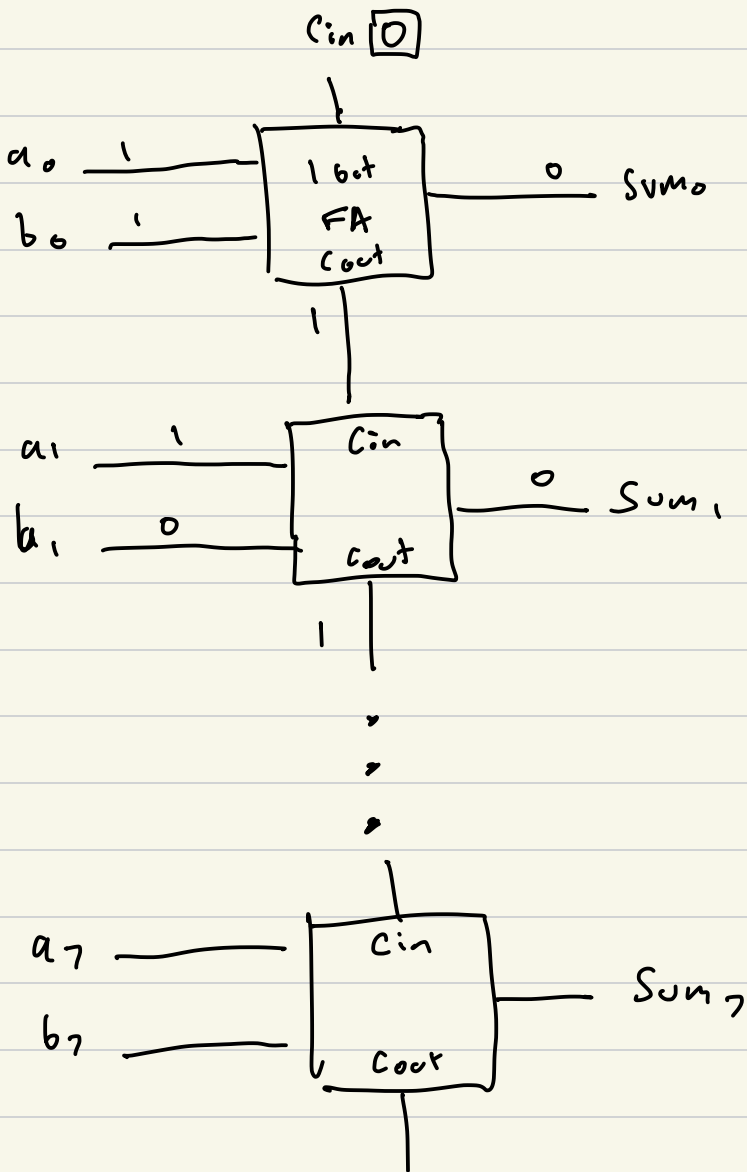

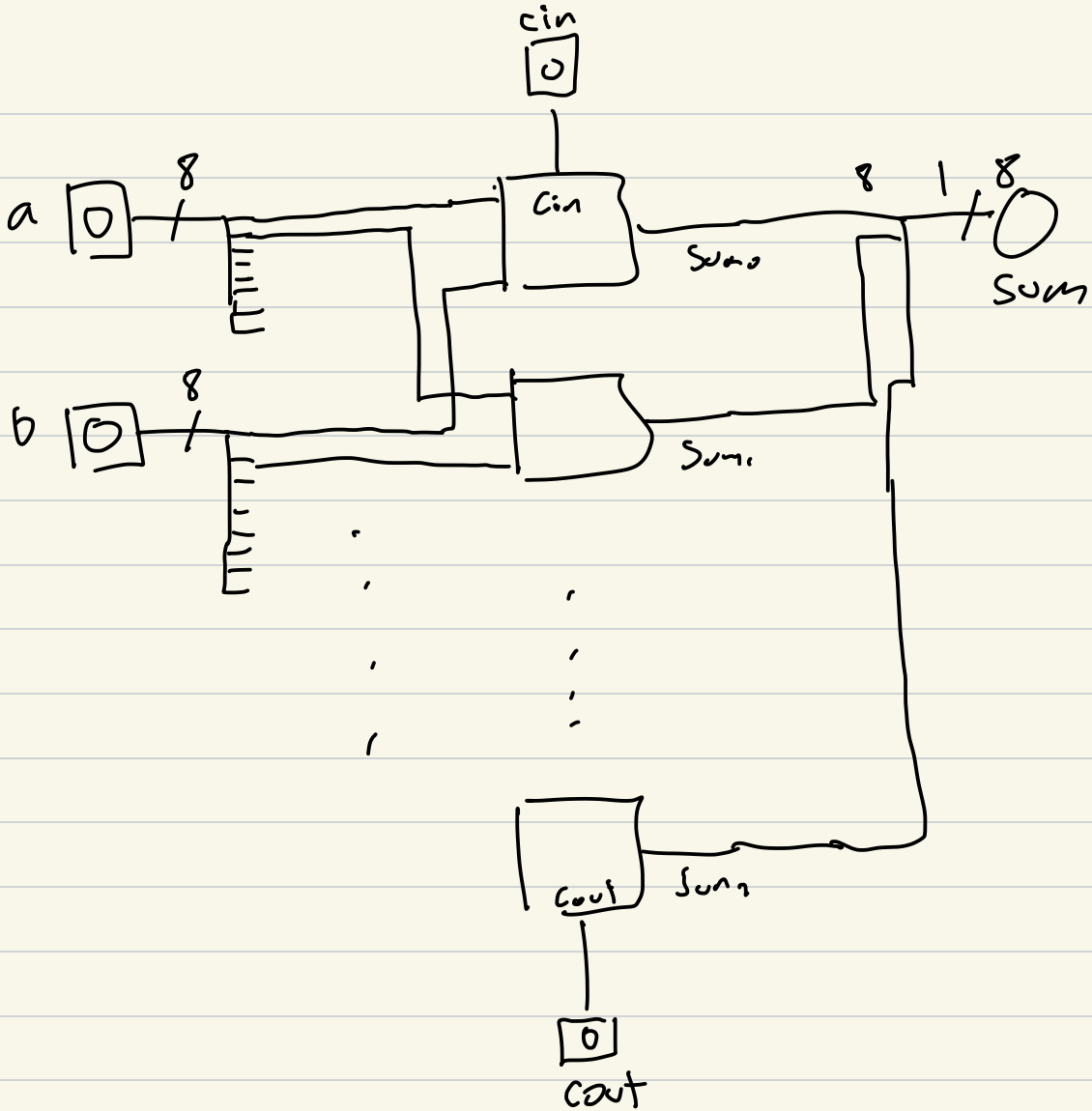
$$\begin{array}{r} 011a \\ + 001b \\ \hline 0 \end{array}$$



Subtraction

$$A - (B)$$


Invert
add 1

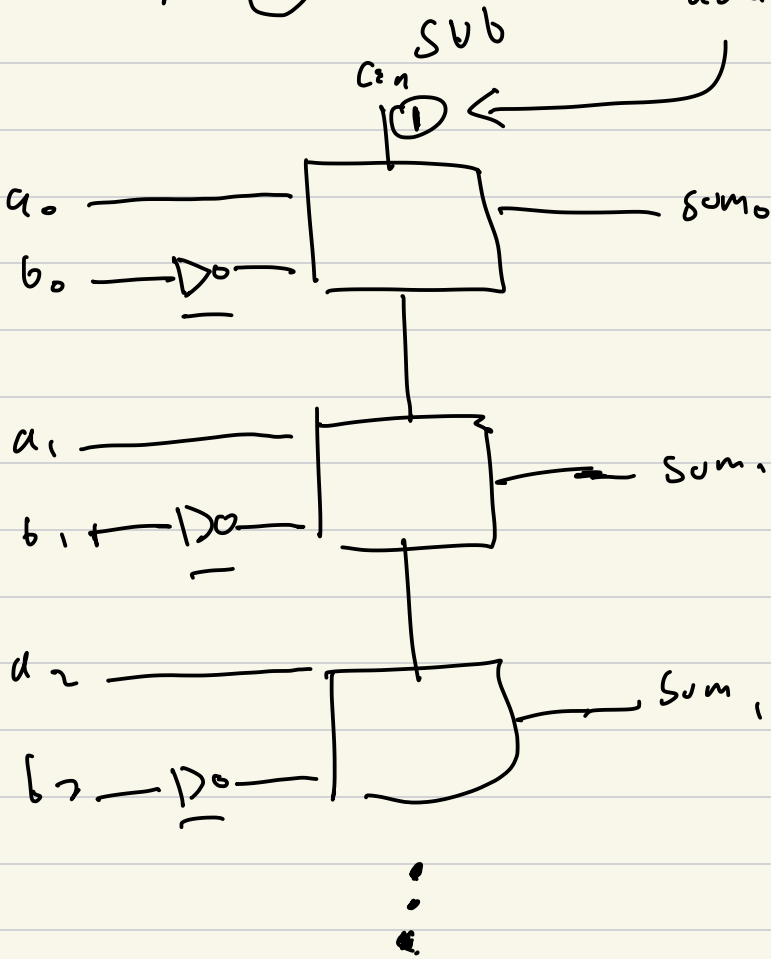

Combinational Logic

components

Multiplexer
Decoders

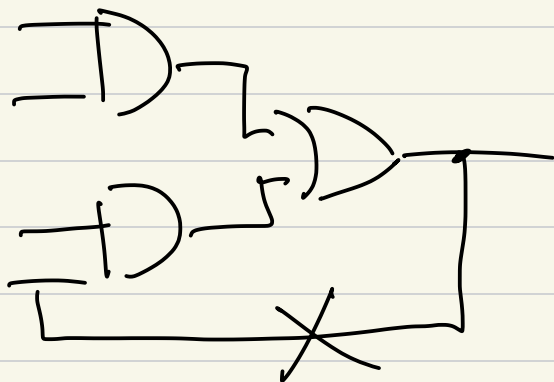


no cycles

Sequential Logic

State

CLOCK

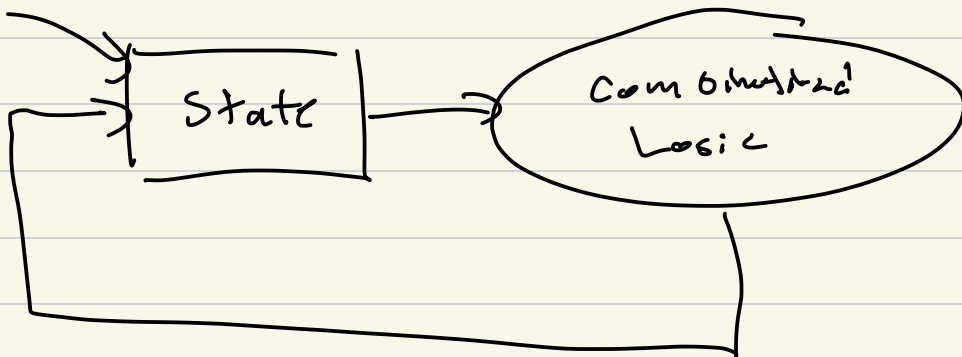

CPU

Autograder on Local Computer (not RISC-V)

autograder

python3

pip3

java

javac