

# CS 315-01 components and Sequential Logic

max 2



$a_1, a_0$	$b_1, b_0$	$r_1, r_0$	$r_i, r_{i+1}$	$r_i, r_{i+1} = (\bar{a}_1 \cdot \bar{a}_0 \cdot \bar{b}_1 \cdot \bar{b}_0) + (\bar{a}_1 \cdot \bar{a}_0 \cdot \bar{b}_1 \cdot b_0) + (\bar{a}_1 \cdot a_0 \cdot \bar{b}_1 \cdot \bar{b}_0) + (\bar{a}_1 \cdot a_0 \cdot \bar{b}_1 \cdot b_0)$
0 0	0 0	0 0	1	
0 0	0 1	0 1	1	
0 0	1 0	1 0	0	
0 0	1 1	1 1	0	
0 1	0 0	0 1	1	$r_1 = \bar{r}_1$
0 1	0 1	0 1	1	
0 1	1 0	1 0	0	
0 1	1 1	1 1	0	
1 0	0 0	1 0	0	
1 0	0 1	1 0	0	
1 0	1 0	1 0	0	
1 0	1 1	1 1	0	
1 1	0 0	1 1	0	
1 1	0 1	1 1	0	
1 1	1 0	1 1	0	
1 1	1 1	1 1	0	


# Project 05

## Combinational Logic

Comparator is  $a == b$  ?


a	b	eq?	XOR	XNOR
0	0	1	0	1
0	1	0	1	0
1	0	0	1	0
1	1	1	0	1

1 bit comparator

 


if (a == b)

2-bit comparator

 


N-bit comparator

8-bit


 


# Multiplexor (MUX)


1 bit 2 input MUX

 

32 bit 2 input MUX

  

ALU

 


# 1 bit 2 input MUX

a	b	s	r
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1




Sum-of-products

$$r = ( \quad ) + ( \quad ) + \dots$$


## Direct implementation

 



1 bit 4 input MUX

   

# 2 bit 2 input MUX

 

# Sequential Logic


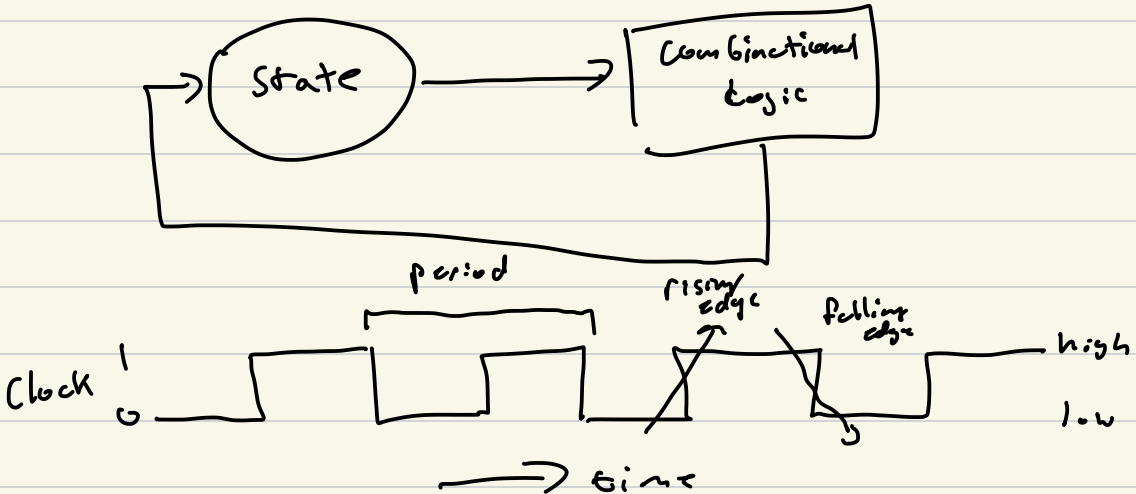
 


DAG


How to store a 1 bit value?

SR Latch set / reset

Static  
RAM

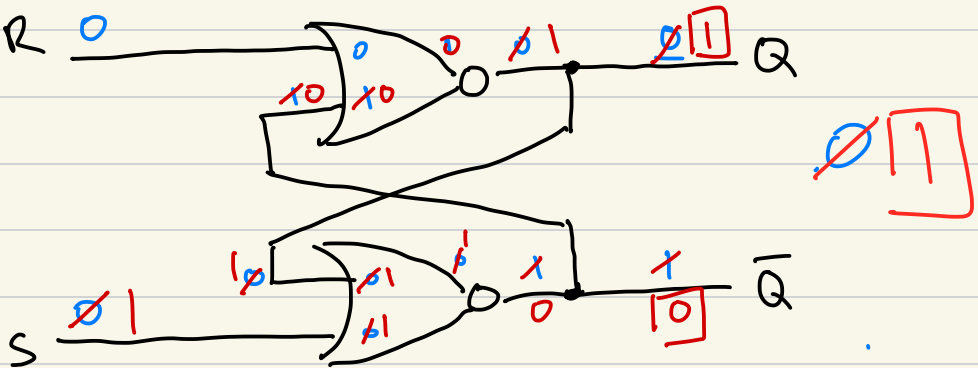 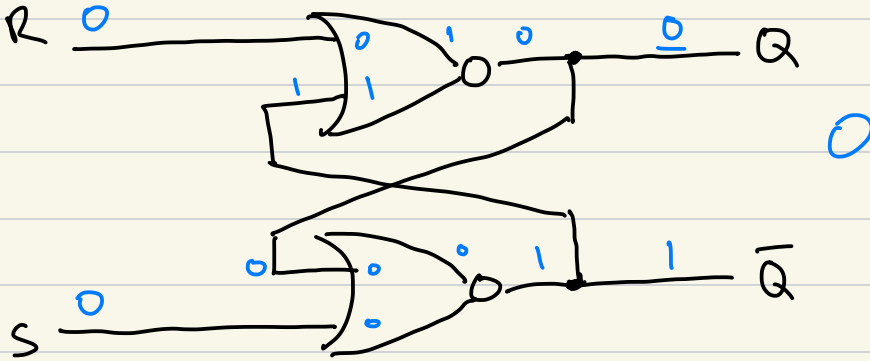



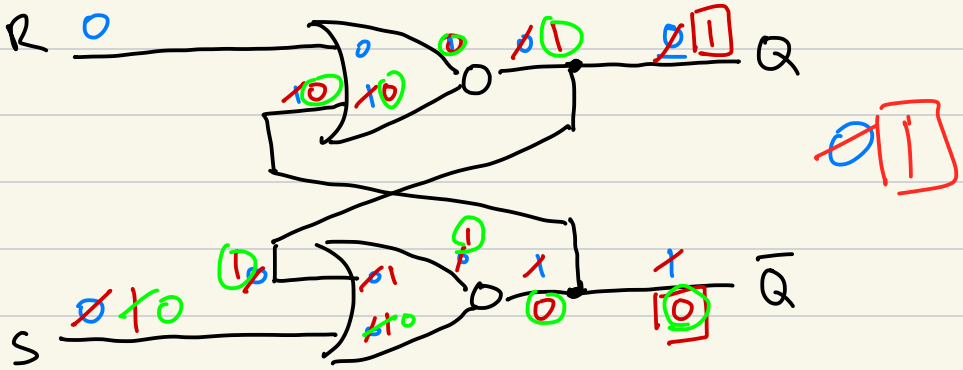

time



R	S	Q	$\bar{Q}$
1	0	0	1
0	0	0	1
0	1	1	0
0	0	1	0
1	1	X	X

undefined