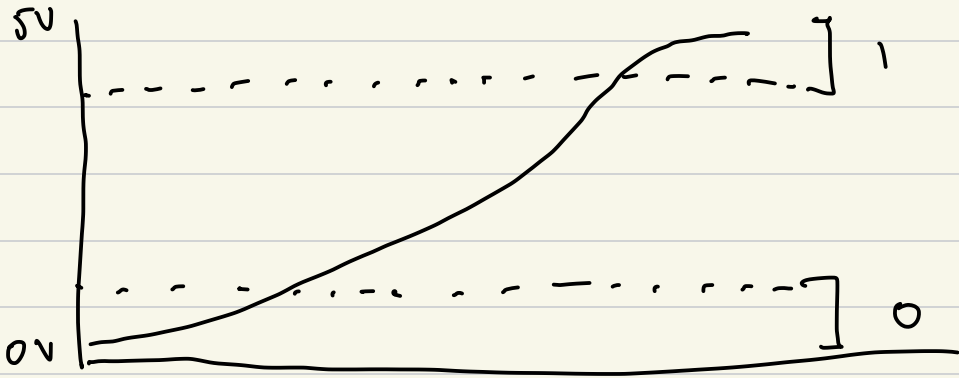


CS 315-02 Lab Intro to Digital Design

Digital Design


Analog \rightarrow Digital



Wires

devices \rightarrow gates

AND

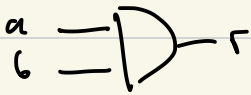

Code $r = a \& b$

boolean algebra $r = a \cdot b$

Logic $r = a \wedge b$

a	b	r
0	0	0
0	1	0
1	0	0
1	1	1

OR



$r = a | b$

$r = a + b$

$r = a \vee b$

a	b	r
0	0	0
0	1	1
1	0	1
1	1	1

NOT




$r = \sim a$

$r = \bar{a}$

$r = \neg a$


a	r
0	1
1	0

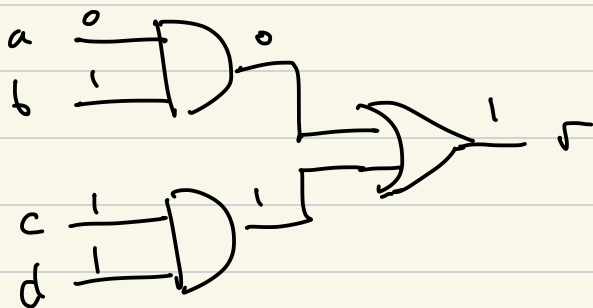

$$r = (a \cdot b) + (c \cdot d)$$

Abstraction

Goal

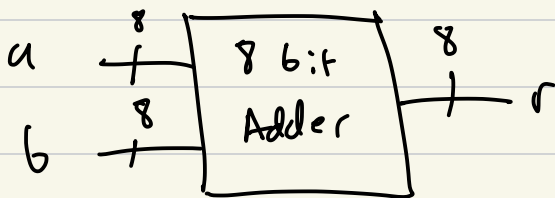

sum-of-products

sum of two 1-bit numbers

C_n

	a	b	sum
	0	0	0
①	0	1	1
②	1	0	1
	1	1	0

XOR sum = $a \oplus b$

$$\text{sum} = (\bar{a} \cdot b) + (a \cdot \bar{b})$$

product term


$a=0 \quad b=1$


$$\begin{aligned} \text{sum} &= (\bar{0} \cdot 1) + (0 \cdot \bar{1}) \\ &= (1 \cdot 1) + (0) \\ &= (1 \cdot 1) \\ &= 1 \end{aligned}$$

$\text{sum} = 0$

$$\text{sum} = (\bar{a} \cdot b) + (a \cdot \bar{b})$$

1	0
0	1

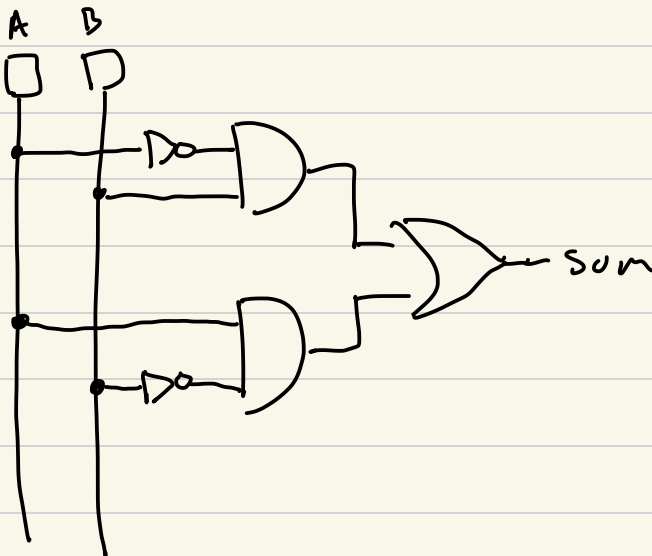

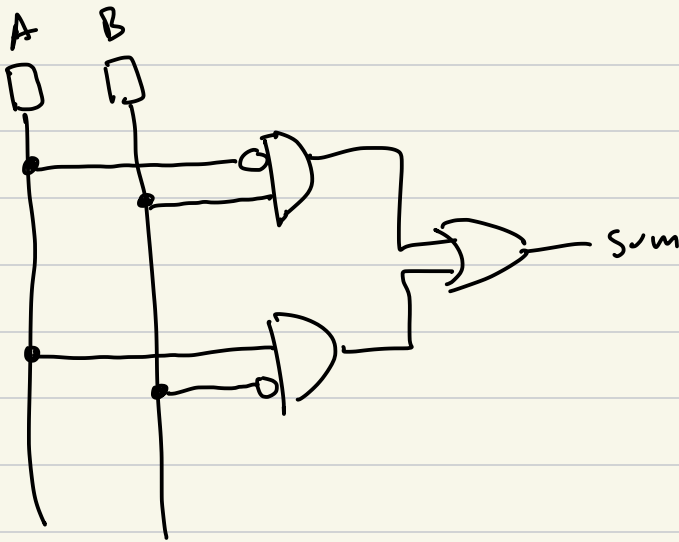

Sum-of-products

1) build truth table

2) Identify rows with output 1


3) Construct product ^(.) terms for each row

a) don't invert if input is 1

b) invert if input is 0

4) Sum (+) all product terms

1 bit full adder

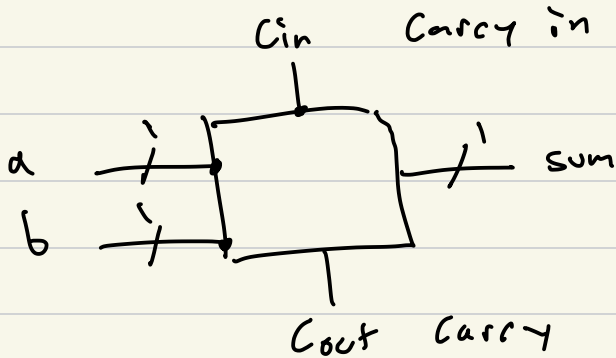

	a	b	Cin	sum	Cout
	0	0	0	0	0
①	0	0	1	1	0
②	0	1	0	1	0
	0	1	1	0	1
③	1	0	0	1	0
	1	0	1	0	1
	1	1	0	0	1
④	1	1	1	1	1

$$\text{sum} = (\bar{a} \cdot \bar{b} \cdot C_{in}) + (\bar{a} \cdot b \cdot \bar{C}_{in}) + (a \cdot \bar{b} \cdot \bar{C}_{in}) + (a \cdot b \cdot C_{in})$$

